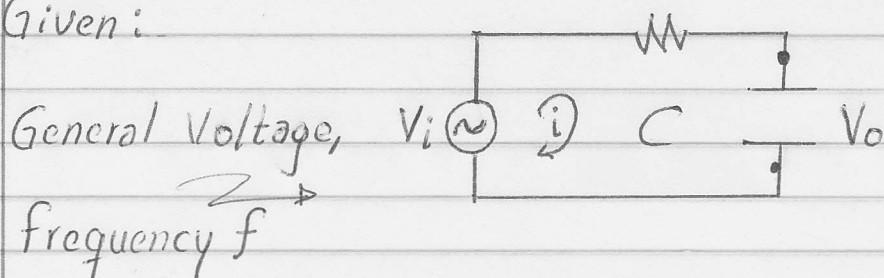


# Linear Circuit Analysis

①

Given:



RC circuit, an input voltage source  $V_i$ , output  $V_o$  of interest.

Find: The transfer function  $H(f) = \frac{V_o(f)}{V_i(f)}$

Solution: Assume waveforms  $V_i(t) = \text{Re}\{\tilde{V}_i(f)e^{j\omega t}\}$

$$V_o(t) = \text{Re}\{\tilde{V}_o(f)e^{j\omega t}\}$$

Where  $j = \sqrt{-1}$ ,  $\omega = 2\pi f$ ,  $f = \text{frequency}$ ,

$$e^{j\omega t} = \cos(\omega t) + j\sin(\omega t)$$

$\tilde{V}_i(f)$  is the complex amplitude of the source waveform,

$$\tilde{V}_i(f) = \tilde{V}_i^{\text{Real}}(f) + j\tilde{V}_i^{\text{Imagi}}(f)$$

Once we know  $H(f)$ , any  $V_i$  and  $V_o$  can be figured

out using  $V_o(t) = \mathcal{F}^{-1}\{\mathcal{F}(V_i(t))H(f)\}$

$\mathcal{F}$  is the Fourier transform operator, and its inverse.


By the convolution theorem we could also write

(2)

$$V_o(t) = V_i(t) \otimes H(t) \quad \leftarrow \begin{array}{l} * \\ \text{Inverse Fourier transform} \\ \text{of } H(f) \end{array}$$

$\otimes$ : convolution operator

What happened to Ohms Law?

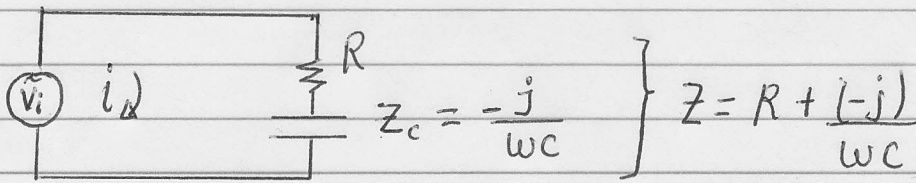

$$\tilde{V}_i = i Z \quad \rightarrow \quad \text{Can calculate } i$$

$$i = \frac{\tilde{V}_i}{Z}$$

Then  $V_R \equiv$  Resistor voltage  $= iR$ ,

$$V_R = \frac{R}{Z} \tilde{V}_i$$

$$\text{Capacitor voltage} \equiv V_C = \frac{Z_c}{Z} \tilde{V}_i$$


This is our normal voltage divider.

That's some fine mathematics.

Where is the physics?

Here.  $i \downarrow \begin{array}{c} \text{Resistor} \\ \text{Voltage} = iR \end{array}$

$$\text{Power dissipated} = V_R i = i^2 R = \frac{V^2}{R}$$

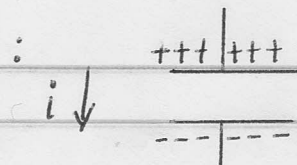And here:   $C = \frac{Q}{V_c} = \text{capacitance}$  (3)

$Q = \text{charge on capacitor}$

$V_c = \text{voltage across capacitor.}$

Suppose we turn on the current  $i$  at time  $t=0$ .

Later the charge piled up on the capacitor is

$$Q(t) = \int_0^t i(\tau) d\tau$$


The capacitor has capacity to hold charge!

Remember,  $i = \frac{dQ}{dt}$  is current.

The voltage across the capacitor is


$$V_c = \frac{Q}{C} = \frac{\int_0^t i(\tau) d\tau}{C}$$

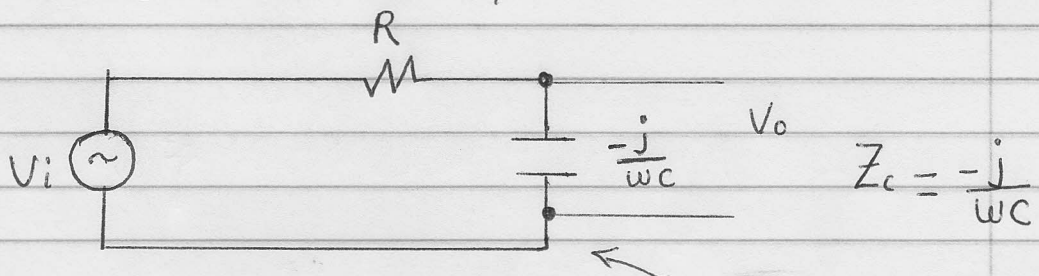This equation says that with a large capacity  $C$  it takes a long time to build up the voltage  $V_c$ .



This is a low pass filter

Low pass filter

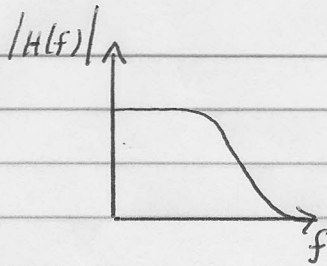

Why?  $Z_c(\omega \rightarrow 0) = \infty$  !

$Z_c(\omega \rightarrow \infty) = 0$  !

It is a simple voltage divider circuit.

$Z_c \gg R$  as  $f \rightarrow 0$ ,  $Z_c \ll R$  as  $f \rightarrow \infty$

Actual transfer function:

$$H(f) = \frac{Z_c}{Z_c + R} = \frac{1}{1 + \frac{R}{Z_c}} = \frac{1}{1 + j\omega RC}$$

The "RC time constant" is  $\tau \equiv RC$

$$H(f) = \frac{1}{1 + 2\pi j f \tau}$$

Complex number.

$ H(f)  = \frac{1}{\sqrt{1 + (2\pi f \tau)^2}}$	Magnitude
Phase $H(f) = -\tan^{-1}(2\pi f \tau)$	

Why a phase shift? It takes time for the capacitor to charge.

$A + f \rightarrow \text{small, e.g. } fT \ll 2\pi,$

$$|H(f)| = 1, \text{ phase} = 0$$

$A + f \rightarrow \infty, \text{ e.g. } fT \gg 2\pi,$

$$|H(f)| \rightarrow 0, \text{ phase} \rightarrow \frac{\pi}{2}$$

The filter has both an effect on the signal amplitude and phase.

Fourier Analysis:


$$\text{Let } V(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} \tilde{V}(f) e^{2\pi f t j} df$$

$$\tilde{V}(f) = \int_{-\infty}^{\infty} v(t) e^{-2\pi f t j} dt$$

Defines a Fourier transform pair

Note:  $e^{2\pi f t j} = \cos(2\pi f t) + j \sin(2\pi f t)$

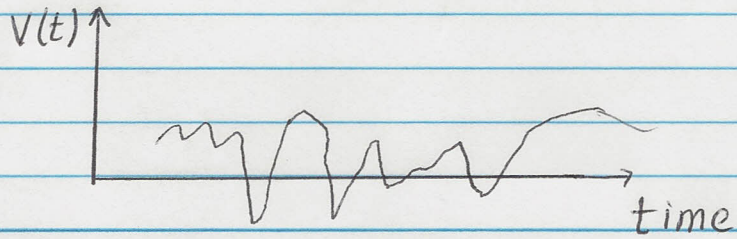(Euler Identity) ↑  
a sine and cosine wave



Physically  $\tilde{V}(f)$  is the superposition of sine and cosine waves needed to reproduce  $V(t)$ .

(6)

Where does  $Z_c = \frac{-j}{\omega C}$  come from?

$$\begin{array}{c} i \downarrow \\ \text{+++} | \text{+++} \\ \text{---} | \text{---} \end{array} \quad i = \frac{dQ}{dt} \quad C = \frac{Q}{V}$$

Transform  $i(t)$  and  $V(t)$  to the frequency domain  $\tilde{i}(f)$ ,  $\tilde{V}(f)$ .

$$Z_c = \frac{\tilde{V}(f)}{\tilde{i}(f)} = \frac{\tilde{Q}(f)}{C \tilde{i}(f)} \dots (1)$$

$$Q(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} \tilde{Q}(f) e^{j2\pi f t} df$$

$$\frac{dQ}{dt} = \frac{1}{2\pi} \int_{-\infty}^{\infty} \tilde{Q}(f) j2\pi f df$$

In other words,

$$i(t) = \frac{dQ}{dt} = \frac{1}{2\pi} \int_{-\infty}^{\infty} \tilde{Q}(f) j2\pi f df$$

$$i(t) = \mathcal{F} \{ \tilde{Q}(f) j 2\pi f \}$$

(7)

Doing  $\mathcal{F} \{ \}$  to both sides,

$$\hat{i}(f) = \tilde{Q}(f) j 2\pi f \dots (2)$$

Using eq.(2) in eq.(1),

$$\Rightarrow \boxed{Z_c = \frac{-j}{2\pi f C} = \frac{-j}{\omega C}}$$

We are working in the frequency domain when we use  $Z_c$ .