



Time Constants 

$$C \equiv \frac{q}{V_c}$$

$$V_R = i R$$

or

$$V_R = \frac{dq}{dt} R$$

$q \equiv$  charge on capacitor

$i \equiv dq/dt =$  current

$V_R = i R$   
(Ohm's Law)

Suppose at  $t=0$  we close the switch.

What are  $V_c(t) + V_R(t)$ ?

Kirchoff's Law:  $V = V_c + V_R$

(1) 
$$V = \frac{q}{C} + R \frac{dq}{dt}$$

Guess a solution:

(2) 
$$q = q_0 (1 - e^{-t/\tau})$$

(3) Note: 
$$\frac{dq}{dt} = \frac{q_0}{\tau} e^{-t/\tau}$$

Use (2) and (3) in (1).

$$V = \frac{q_0}{C} (1 - e^{-t/\tau}) + \frac{R q_0}{\tau} e^{-t/\tau}$$

Boundary Conditions:  $t \rightarrow \infty, q_0 = C \cdot V$  (Capacitor is charged)

$t \rightarrow 0, V = \frac{RCV}{\tau} \therefore$

$$\tau = RC$$

Time Constant

$$V_c(t) = V (1 - e^{-t/\tau})$$

$$V_R(t) = V e^{-t/\tau}$$

